

Reducing Ringing Through PCB Layout Techniques

David Jauregui

PMP - Power Stage

ABSTRACT

Designers must consider several topics when designing a printed-circuit board (PCB) layout for a dc-to-dc converter. In particular, the layout of the Power Stage components within a nonisolated synchronous buck converter requires special attention in order to optimize the overall performance of the switching function. The Power Stage in this application report is defined to include the input capacitors, power MOSFETs, driver IC, and output inductor (see [Figure 1](#)).

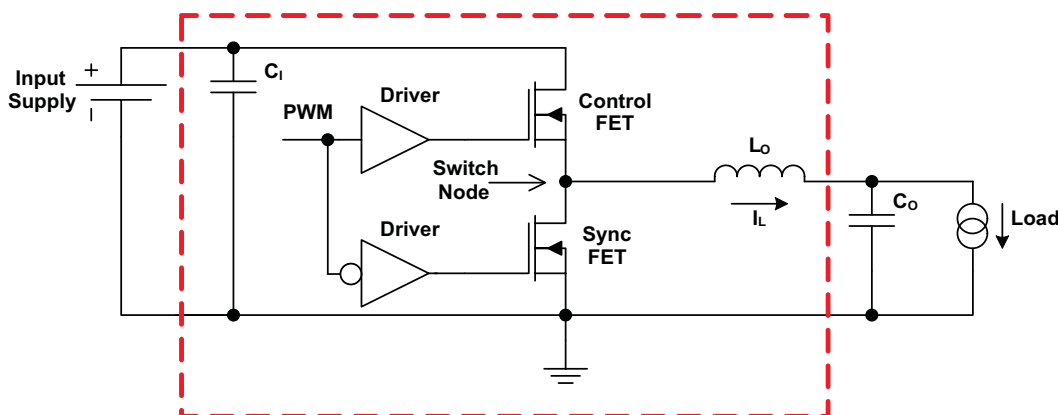


Figure 1. Definition of Power Stage Components

This document discusses the topic of *voltage ringing* commonly found to be superimposed on the *rising edge* of the switch node (V_{SW}) waveform. It also describes how to optimize the PCB layout design to minimize the magnitude of the ringing.

Background

The two major industry concerns toward the ringing commonly found to be superimposed on the switch node waveform are:

1. Voltage Margin
 - This is a percentage ratio which takes the magnitude of the first peak within the ringing waveform and compares it to the breakdown voltage of the power MOSFET (BV_{DSS}).
2. EMI/EMC
 - This the amount of conducted or radiated noise produced by the ringing waveform.

This application report only addresses the topic of voltage margin and does not focus on the topic of EMI/EMC. The topic of EMI/EMC can be somewhat subjective and greatly depends on the overall system/chassis design. However, the enhancements outlined in this document can improve the overall EMI/EMC performance of the system.

In terms of voltage margin, designers occasionally impose an 80% margin rule. This means that the maximum voltage measured across the drain to source of any MOSFET must not exceed 80% of the MOSFET's BV_{DSS} . For example, a MOSFET with a $BV_{DSS} = 25\text{ V}$ requires only 20 V applied across the device at any given time. As such, power supply designers need to have a solution to address a situation that yields ringing that may exceed their voltage margin requirements.

Optimized Placement of Power Stage Components

The Control FET has the ability to switch voltages at rates greater than 10 kV/ μs . Special care must be taken with the PCB layout design and placement of the Power Stage components in order to minimize voltage ringing at the switch node of this topology. Of particular importance is the placement of the input capacitors relative to the power MOSFETs. It is important to minimize the node lengths between these components.

1. Minimize the node length between the positive terminal of the input capacitors and the Drain pin of the Control FET.
2. Minimize the node length between the negative terminal of the input capacitors and the Source pin of the Sync FET.

A traditional placement of the Power Stage components is shown in Figure 2. Typically, one of these two node lengths is compromised. This results in a higher parasitic inductance between the power MOSFETs and the input capacitors which may yield higher than expected voltage ringing on the switch node. An optimized placement of the Power Stage components is shown in Figure 3. Both node lengths have been minimized which in turn minimizes the parasitic inductances.

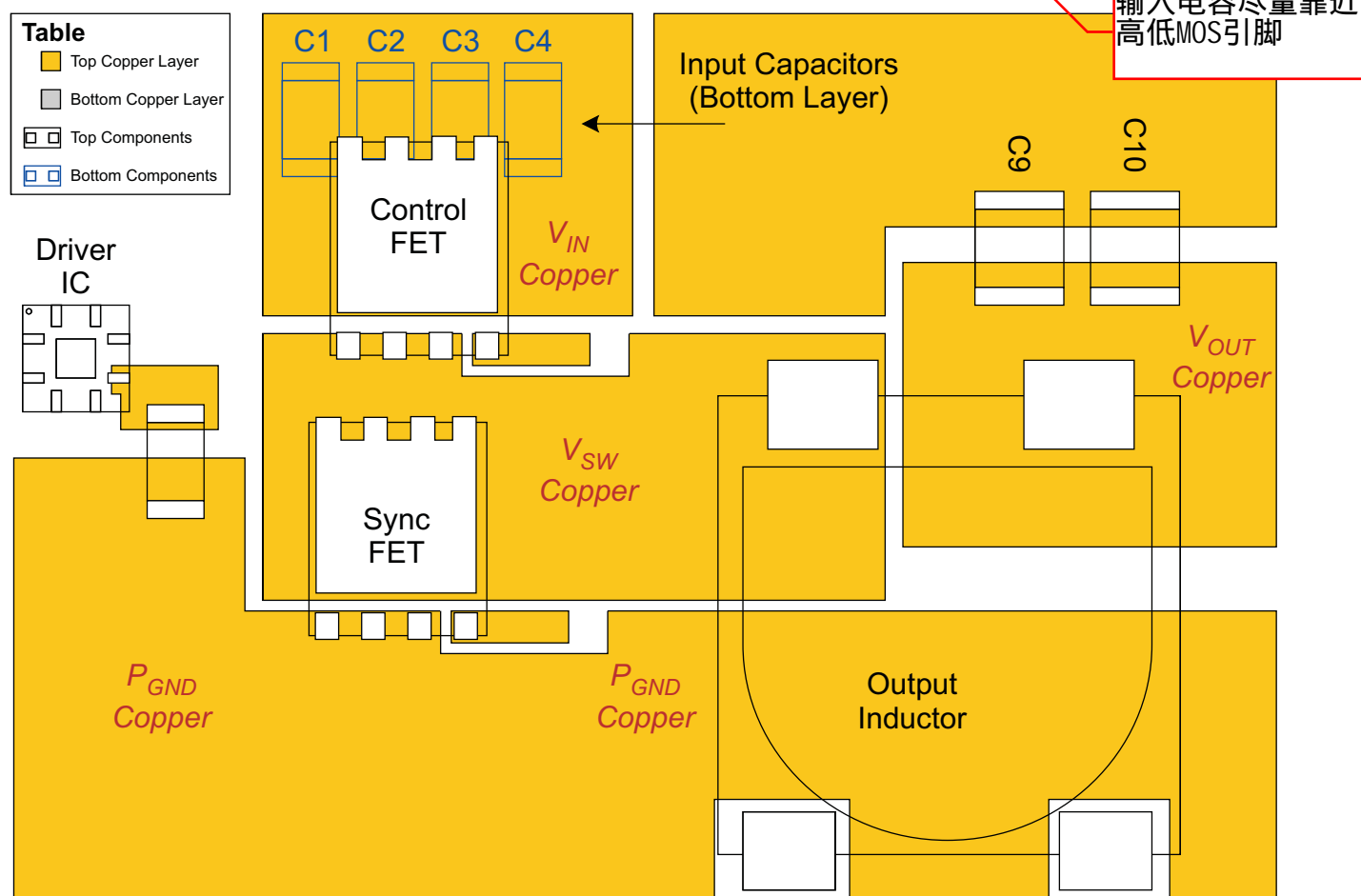


Figure 2. Typical Placement and PCB Layout of the Power Stage Components

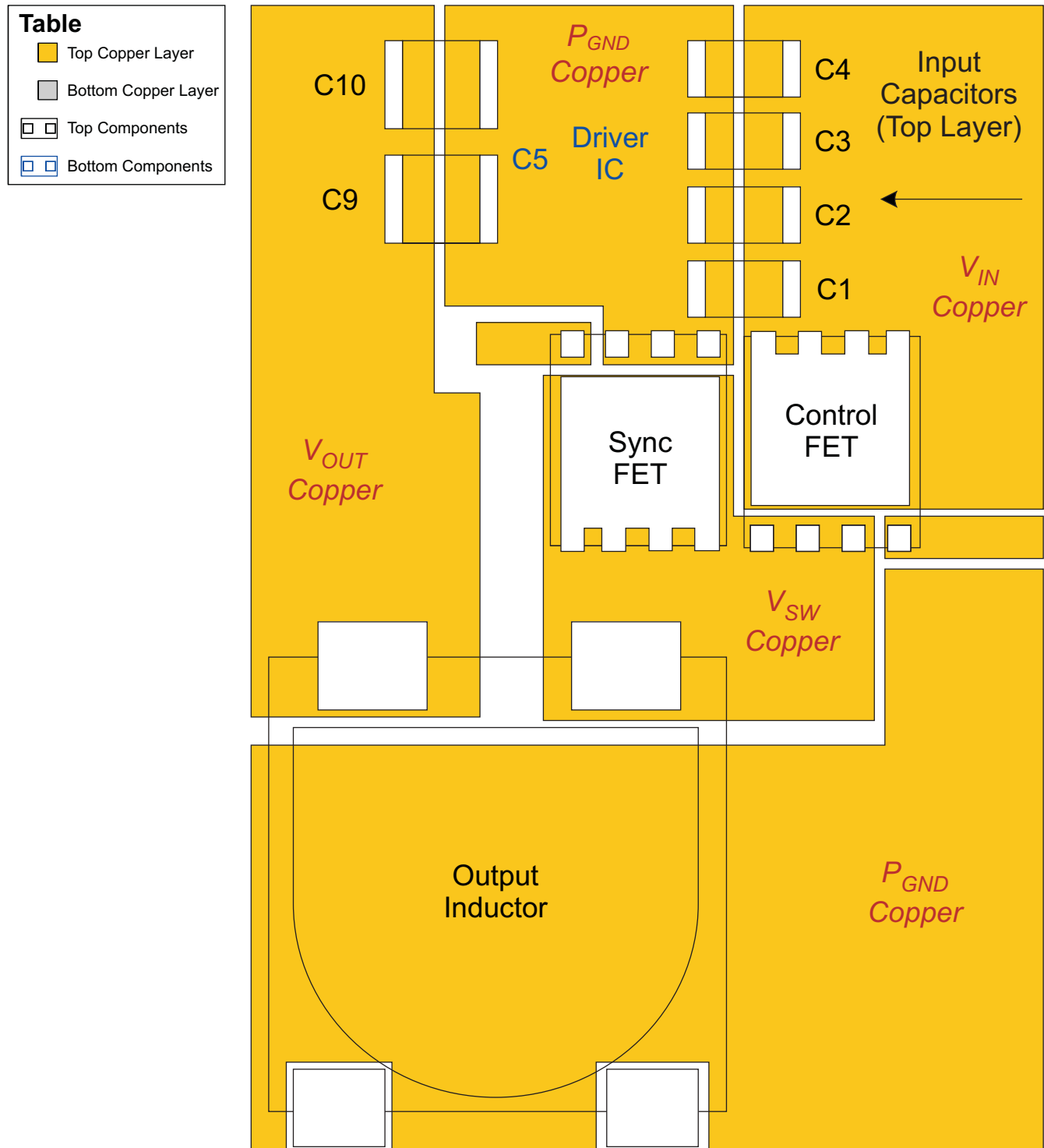


Figure 3. Optimized Placement and PCB Layout of Power Stage Components

The most important difference between Figure 2 and Figure 3 is the distance between the input capacitors and the power MOSFETs. In Figure 3, the Sync FET has been rotated 180° and placed to the left of the Control FET. The input capacitors have been moved to the top layer and placed next to the Drain pins of

the Control FET and the Source pins of the Sync FET. In both examples, ceramic input capacitors were used due to the inherently low equivalent series inductance (ESL) of these types of capacitors (10 μ F, 16 V, 1206, X5R, TDK C3216X5R1A106M). In addition, the optimized layout allows the placement of the driver IC to be put directly below the power MOSFETs on the bottom layer. This minimizes the distance of gate drive traces.

Testing of Layouts

Figure 4 shows the ringing found on the switch node of the PCB layout example depicted in Figure 2. In this example, the amplitude of the ringing reaches 25 V. If the power MOSFETs used in this example were rated for 25 V (BV_{DSS}), then the amplitude of the voltage ringing yields no design margin as outlined in item 1 in the Background section of this document. Figure 5 shows the ringing found on the switch node of the PCB layout example depicted in Figure 3. In this example, the amplitude of the ringing reaches 20 V. By simply optimizing the placement of the power MOSFETs and input capacitors, the voltage ringing amplitude can be reduced by 5 V. If this design used 25-V rated power MOSFETs, the amplitude of the voltage ringing waveform meets the typical margin requirements.

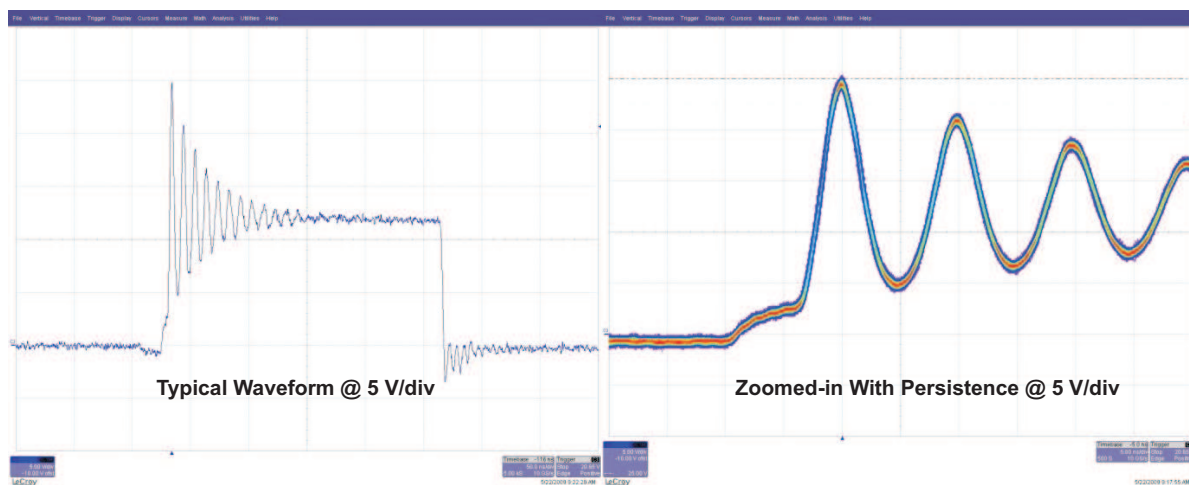


Figure 4. Switch Node (VSW) Voltage Ringing on Typical Layout

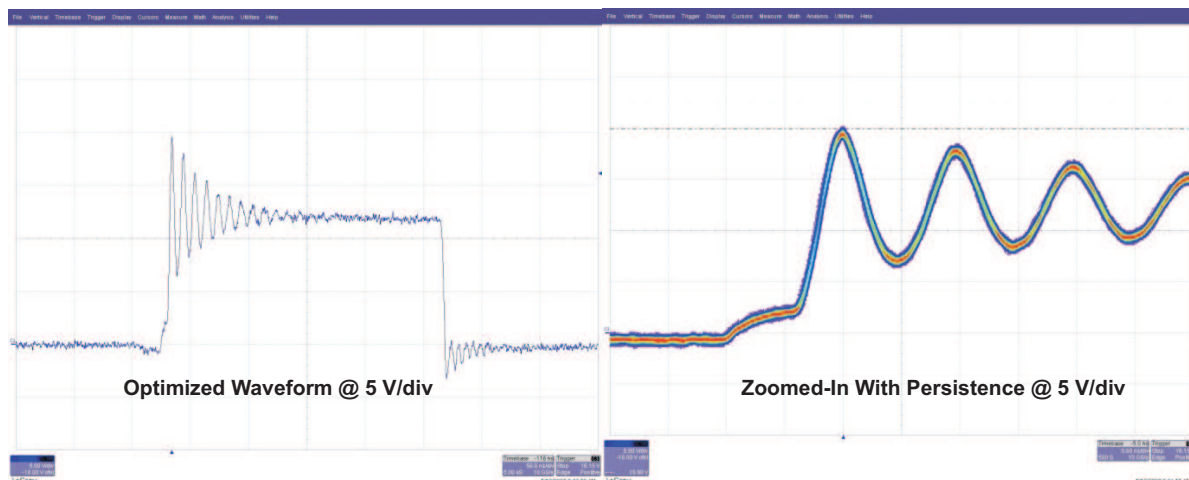


Figure 5. Switch Node (VSW) Voltage Ringing on Optimized Layout

Measurement Techniques

It is important to accurately measure the voltage applied across any power MOSFET in an application. The voltage measurement across the synchronous MOSFET's Drain and Source terminals (the switch node) is particularly important because the high rate of change in voltage imposed by the switching MOSFET induces a certain level of voltage ringing. The peak values of this voltage ringing may be misinterpreted if not properly measured. The following measurement tips can help minimize the overall measurement error.

1. The ground lead length of an oscilloscope probe is the most important item in properly capturing the peak values of the switch node voltage ringing. Do not use the standard 3-inch long ground wire supplied with the oscilloscope probe. The long wire loop will act as an antenna by picking up any radiated noise emitted by the system board and will yield a higher value of switch node voltage ringing than what is actually seen by the device (see [Figure 6](#) and [Figure 7](#)). Instead, use a small-length ground wire that attaches to the oscilloscope probe tip end (see [Figure 8](#)).
2. Placement of the oscilloscope tip and ground must be right on the MOSFET leads. Placement anywhere else introduces higher voltage ringing induced by the PCB parasitic inductance.

A combination of these measurement tips can yield a proper measurement of the actual voltage ringing seen by the synchronous MOSFET.

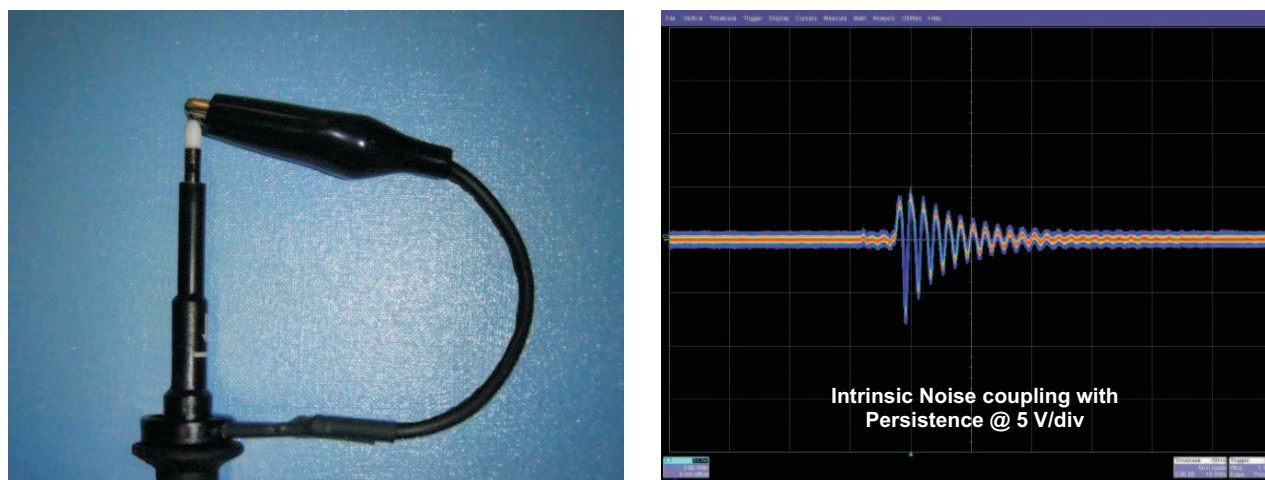


Figure 6. Ringing Voltage Pick-up by 3-Inch Ground Wire

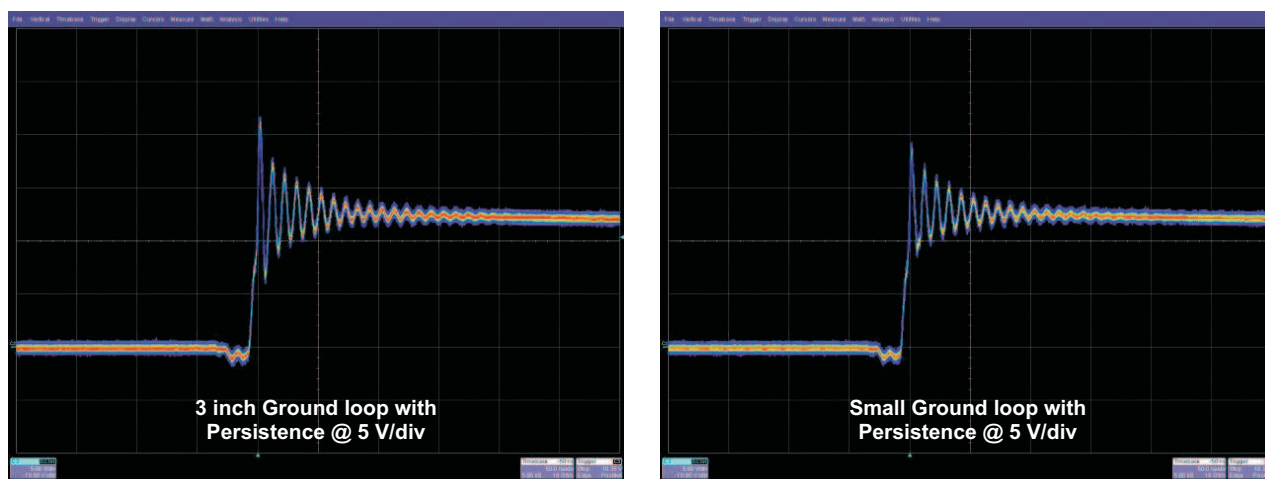


Figure 7. Switch Node Voltage Ringing Measurements: Typical 3-Inch Wire (Left) Versus Small Length Wire (Right)



Figure 8. Oscilloscope Probe Comparison: Typical 3-Inch Wire (Left) Versus Small Length Wire (Right)

Conclusion/Summary

The layout and placement of the Power Stage components in a nonisolated synchronous buck converter requires special attention in order to optimize the overall performance of the switching function. In particular, voltage ringing commonly found to be superimposed on the switching node can be reduced by up to 20% by simply optimizing the placement and PCB layout of the power MOSFETs and input capacitors.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
RF/IF and ZigBee® Solutions	www.ti.com/lprf

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital Control	www.ti.com/digitalcontrol
Medical	www.ti.com/medical
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2009, Texas Instruments Incorporated